

Determination of Voltage in circuit using Nodal Analysis


Aim:-

To determine the voltage in the circuit using nodal analysis both theoretically and practically for a given DC circuit.

Apparatus Required :-

S.No	Apparatus	Specification	Quantity
1	RPS	(0-30)V	1
2	Multimeter	-	3
3	Resistor	470 Ω , 330 Ω	3, 2
4	Bread board	-	1

Circuit Diagram :-

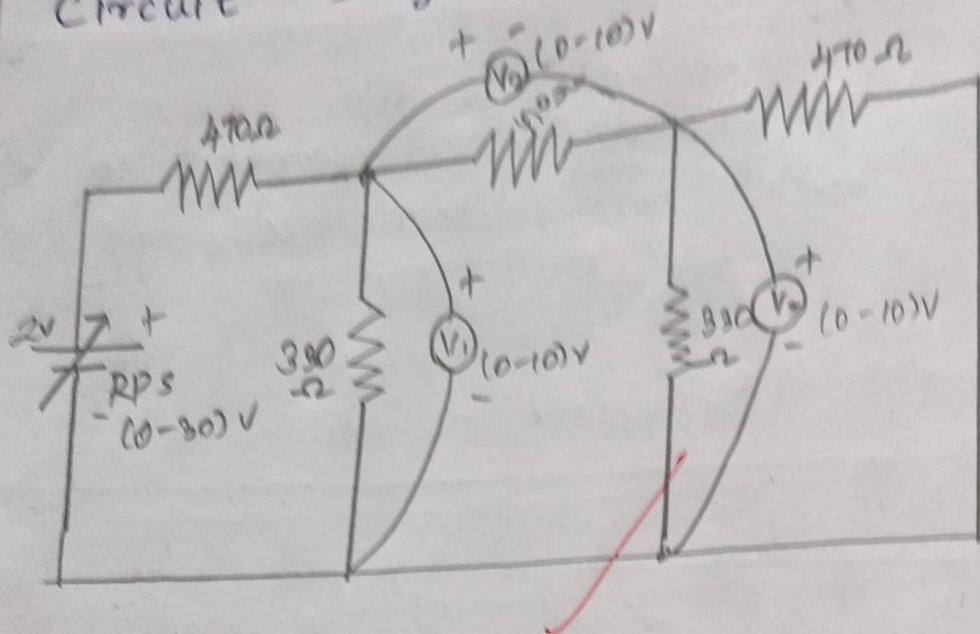

Observation :-

S.No Parameter RPS(volts)	Theoretical Value			practical value		
	V_A	V_B	$V_A - V_B$	V_A	V_B	$V_A - V_B$
2	0.65	0.2	0.45	0.69	0.2	0.48
4	1.27	0.37	0.9	1.33	0.39	0.9
6	1.91	0.55	1.35	2.0	0.68	1.4
8	2.6	0.8	1.8	2.61	0.77	1.86

Calculation :-

$$\frac{V_A - 2}{470} + \frac{V_A}{330} + \frac{V_A - V_B}{470} = 0 \rightarrow \textcircled{1}$$

$$\frac{V_B - V_A}{470} + \frac{V_B}{330} + \frac{V_B}{470} = 0 \rightarrow \textcircled{2}$$

By solving $\textcircled{1}$ & $\textcircled{2}$,

$$V_A = 0.65$$

$$V_B = 0.20$$

$$V_A - V_B = 0.45$$

2.1k

$$\frac{9}{10}$$

RESULT :-

- i) Voltage (V_1) = 0.65
 - ii) Voltage (V_2) = 0.45
 - iii) Voltage (V_3) = 0.2
- } for ($R_{P4} = 2V$)